

---

**Chapter 6**

(6.1)

“bar” is latched. Recode the design to remove the latch as follows.

```

always@(foo or fred)
if (foo == 2'h2) bar = fred;
else bar = 1'bx;
  
```


(6.2)

“fred” and “mike” are latched. Recode the design to remove the latches as follows.

```

always@(foo or hal or tron)
begin
  fred = 1'bx;
  mike = 1'bx;
  case (foo)
    2'b00 : fred = hal;
    2'b01 : fred = tron;
    2'b10 : mike = hal;
    2'b11 : mike = tron;
  endcase
end
  
```

(6.3)

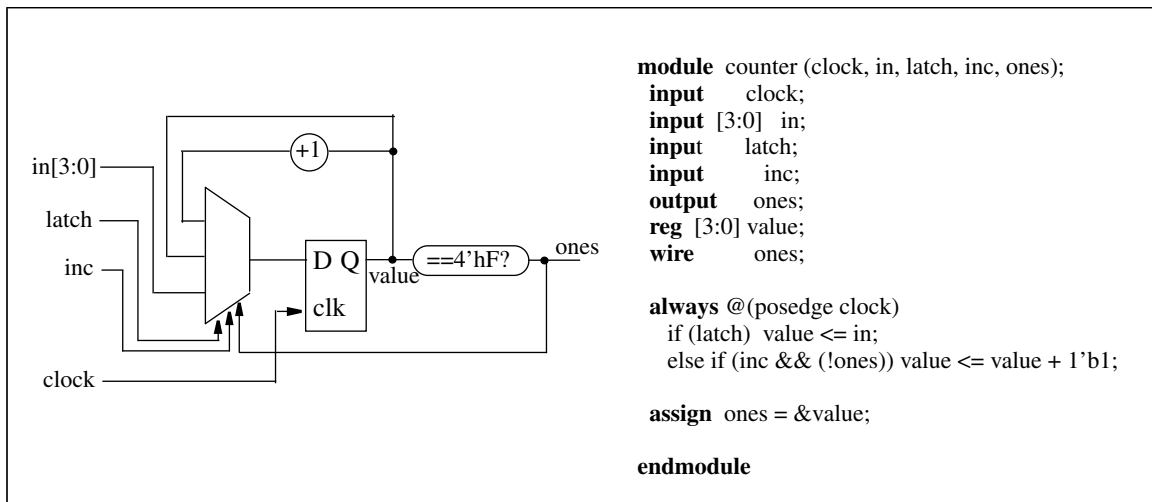

(6.4)

a. See part b.

---

b.

```

reg [4:0] addressA;
reg    zero;

always @(posedge clock)
    AddressA = AddressA + 1'b1;

always @(posedge clock)    // RS flip-flop
    if (data == 32'b0) zero = 1;
    else if (AddressA=5'b0) zero = 0;

```

(6.5)

```

module counter (clock, in, latch, dec, divide-by-two, zero);

input    clock;    /* clock */
input [7:0] in;    /* input initial count */
input    latch;    /* `latch input' */
input    dec;      /* decrement */
input    divide-by-two; /* divide by 2 when high */

output    zero;    /* zero flag */

reg [7:0] value;    /* current count value */
wire    zero;

always @(posedge clock)
begin
    if (latch) value <= #1 in;
    else if (dec && !zero) value <= #1 value - 1'b1;
    else if (divide-by-two) value <= value >> 1;
end

assign zero = ~|value;

endmodule

```

(6.6)

```

module count_compare (clock, in1, in2, in3, load1, load2, dec1, dec2,
count1, count2, ended);

input    clock;
input [7:0] in1, in2, in3;
input    load1; // when load1 goes high, in1 is registered into count1
input    load2; // when load2 goes high, in2 is registered into count2
input    dec1; // decrement count1 by 1
input    dec2; // decrement count2 by in3
output [7:0] count1; // contents of counter 1
output [7:0] count2; // contents of counter 2
output    ended; // goes high when count1=count2, or either counter
                // experiences an unsigned overflow

```

```

((6.6) continued)
// note: count1 and count2 will not change after same goes high until
// load1 or load2 forces one of the to be reloaded.

reg [7:0] count1, count2;
reg [7:0] next_count1, next_count2;
reg      carry1, carry2;
reg      carry1a, carry2a;
wire     ended;

always @(posedge clock)
  if (load1) {carry1a, count1} <= {1'b0, in1};
  else if (dec1 & !ended) {carry1a, count1} <= {carry1, next_count1};

always @(count1)
  {carry1, next_count1} = count1 - 1'b1;

always @(posedge clock)
  if (load2) {carry2a, count2} <= {1'b0, in2};
  else if (dec2 & !ended) {carry2a, count2} <= {carry2, next_count2};

always @(count2)
  {carry2, next_count2} = count2 - in3;

assign ended = (count1 == count2) | carry1a | carry2a;

endmodule

```

(6.7)

```

module IntervalCounter (clock, Data, Interval, Overflow);

input clock;
input [7:0] Data;
output [7:0] Interval;
output Overflow;

reg[7:0] Interval;
reg Overflow;

always@(posedge clock)
  begin
    Interval <= nextInterval;
    Overflow <= nextOverflow;
  end

always@(Data or Interval)
  if (data[7:5] == 4'hF) {nextOverflow, nextInterval} = 9'h1;
  else {nextOverflow, nextInterval} = Interval + 1'b1;

endmodule

```

(6.8)

```
module DataPort (Clock, Reset, Clear, InData, Payload, Count, Error);

input Clock, Reset, Clear;
input [11:0] InData;
output [3:0] Payload;
output [7:0] Count, Error;

reg[3:0] Payload, nextPayload;
reg [7:0] Count, Error, nextCount, nextError;

wire parity;

always@(posedge Clock)
begin
    Payload <= nextPayload;
    Count <= nextCount;
    Error <= nextError;
end

always@(InData or Reset or Clear or Count)
if (!Reset || Clear)
    begin
        nextPayload = 4'h0;
        nextCount = 8'h0;
        nextError = 8'h0;
    end
else if (InData[11:8] == 4'h1)
    begin
        nextPayload = InData[7:4];
        nextCount = Count + 1'b1;
        if (parity != InData[0]) nextError = Error + 1'b1;
        else nextError = Error;
    end
else
    begin
        nextPayload = Payload;
        nextCount = Count;
        nextError = Error;
    end

assign parity = ~^InData[7:4];

endmodule
```

(6.9)

```
module parityCount(clock, data_in, go, odd, even);

input clock;
input [7:0] data_in;
input go;
output [7:0] odd;
output [7:0] even;

wire OddParity;
reg [7:0] odd, even, next_odd, next_even;
```

```

( (6.9) continued )
always@(posedge clock)
begin
    odd <= next_odd;
    even <= next_even;
end

always@(odd or even or OddParity or go)
if (go == 1'b0)
    begin
        next_odd = 8'b0;
        next_even = 8'b0;
    end
else
    begin
        if (OddParity == 1'b1)
            begin
                next_even = even;
                next_odd = odd + 1;
            end
        else
            begin
                next_even = even + 1;
                next_odd = odd;
            end
    end

assign OddParity = ^data_in;

endmodule

```

(6.10)

```

The Verilog module: "exercise610.v"
module AccumStats (clock, reset, clear, DataIn1, DataIn2, EvenParity, GreyCode, overflow);

input clock;    // Clock
input reset;    // synchronous reset (active low)
input clear;    // Clears statistics when high (synchronous)
input [7:0] DataIn1; // Input Data 1
input [7:0] DataIn2; // Input Data 2

// all outputs are registered
output [7:0] EvenParity; // # of data with Even parity
output [7:0] GreyCode; // # of data with pattern 10101010 or 01010101
output overflow; // =1 if any of the counters above overflow

reg [7:0] EvenParity, GreyCode;
reg overflow;

reg [7:0] NextEvenParity, NextGreyCode;
reg CarryOutParity, CarryOutGrey;

```

```

( (6.10) continued)
always@(posedge clock)
  if (!reset || clear) EvenParity <= 8'd0;
  else EvenParity <= NextEvenParity;

always@(posedge clock)
  if (!reset || clear) GreyCode <= 8'd0;
  else GreyCode <= NextGreyCode;

always@(posedge clock)
  if (!reset || clear) overflow <= 1'd0;
  else overflow <= CarryOutParity | CarryOutGrey;

always@(EvenParity or DataIn1 or DataIn2)
  case ({~^DataIn1, ~^DataIn2}) // synopsys full_case parallel_case
    2'b01 : {CarryOutParity, NextEvenParity} = EvenParity + 1'b1;
    2'b10 : {CarryOutParity, NextEvenParity} = EvenParity + 1'b1;
    2'b11 : {CarryOutParity, NextEvenParity} = EvenParity + 2'd2;
    default : {CarryOutParity, NextEvenParity} = {1'b0, EvenParity} ;
  endcase

always@(GreyCode or DataIn1 or DataIn2)
  {CarryOutGrey, NextGreyCode} = GreyCode +
    ((DataIn1 == 8'b10101010) | (DataIn1 == 8'b01010101)) +
    ((DataIn2 == 8'b10101010) | (DataIn2 == 8'b01010101));

endmodule

```

The testbench file is as follows:

```

'include "exercise610.v"

module test_fixture;

  parameter TestCycles = 260; // # test cycles
  parameter TC = 10; // # Clock period in ns

  reg clock;
  reg reset, clear;
  reg [7:0] DataIn1 Vectors [TestCycles-1:0];
  reg [7:0] DataIn2 Vectors [TestCycles-1:0];

  reg [7:0] ExpectedEvenParity [TestCycles-1:0];
  reg [7:0] ExpectedGreyCode [TestCycles-1:0];
  reg [TestCycles-1:0] ExpectedOverflow;

  reg [7:0] DataIn1;
  reg [7:0] DataIn2;
  wire overflow;
  wire [7:0] EvenParity, GreyCode;

  integer i,j;

  initial // setup vectors
  begin
    DataIn1 Vectors [0] = 8'h03;
    DataIn1 Vectors [1] = 8'hAA;
    DataIn1 Vectors [2] = 8'h03;
    DataIn1 Vectors [3] = 8'h03;
  end

```

```

DataIn2Vectors [0] = 8'h03;
DataIn2Vectors [1] = 8'h01;
DataIn2Vectors [2] = 8'h01;
DataIn2Vectors [3] = 8'h01;

ExpectedEvenParity [0] = 8'h02;
ExpectedEvenParity [1] = 8'h03;
ExpectedEvenParity [2] = 8'h04;
ExpectedEvenParity [3] = 8'h05;

ExpectedGreyCode [0] = 8'h0;
ExpectedGreyCode [1] = 8'h1;
ExpectedGreyCode [2] = 8'h1;
ExpectedGreyCode [3] = 8'h1;

ExpectedOverflow [0] = 8'h0;
ExpectedOverflow [1] = 8'h0;
ExpectedOverflow [2] = 8'h0;
ExpectedOverflow [3] = 8'h0;

for (i=4; i<=TestCycles-1; i = i+1)
  begin
    DataIn1 Vectors [i] = 8'h03;
    DataIn2 Vectors [i] = 8'h01;
    {ExpectedOverflow[i], ExpectedEvenParity [i]} = ExpectedEvenParity[i-1] + 1'b1;
  end
end

initial //the following block executed only once
begin
$shm_open("waves.shm");
$shm_probe("AS");

// insert monitor statement here
$monitor("Time =%d; Clock = %b; DataIn1 = %h; Evenparity = %h; GreyCode = %h",
  $stime, clock, DataIn1, EvenParity, GreyCode);

  clock = 0;
  reset = 1;
  clear = 0;
  #6 DataIn1 = 8'h01;
  DataIn2 = 8'h01;
  #TC clear = 1;
  #TC clear = 0;
  #TC for (j=0; j<=TestCycles-1; j = j+1)
    begin
      DataIn1 = DataIn1 Vectors[j];
      DataIn2 = DataIn2 Vectors[j];
      #TC
      if (EvenParity != ExpectedEvenParity[j])
        $display("Error in Parity cycle %d\n", j);
      if (GreyCode != ExpectedGreyCode[j])
        $display("Error in Grey Code\n");
      if (overflow != ExpectedOverflow[j])
        $display("Error in Overflow \n");
    end
  $shm_close(); //closes data base
$finish;
end

always #5 clock=~clock; //10ns clock

AccumStats u1 (clock, reset, clear, DataIn1, DataIn2, EvenParity, GreyCode, overflow);

endmodule /* test_fixture */

```

(6.11)

```

module SaturatingAccumulator (clock, go, in, out);

input clock;
input go; // Accumulate inputs while go is high, clear when low
input [7:0] in;
output [7:0] out;
wire Cout, zero, saturate;
wire [7:0] Sum;
reg [7:0] out, next_out;
reg [2:0] count, next_count;

assign {Cout, Sum} = out + in;

always@(posedge clock)
    out <= next_out;
always@(in or go or zero or Cout or Sum)
    casex({go, zero, Cout, saturate})
        4'b0xxx : next_out = 8'b0;
        4'b11xx : next_out = in;
        4'b101x : next_out = 8'hFF;
        4'b10x1 : next_out = 8'hFF;
        default : next_out = Sum;
    endcase
always@(posedge clock)
    count <= next_count;
always@(go or count)
    if (go==0) next_count = 3'h0;
    else next_count = count + 1'b1;

assign zero = (count == 0);
assign saturate = (out == 8'hFF);
endmodule

```

(6.12)

Latches are accidentally inferred; incomplete sensitivity list; “casex” should be used.

```

reg [1:0] Sel2;
reg in1, in2, out1, out2;

always@ (in1 or in2 or Sel2)
begin
    out1 = in2;
    out2 = in1;
    casex (Sel2)
        2'b1x : begin out1 = in1; out2 = in2; end
        default : ;
    endcase
end

```



---

**Chapter 7**

(7.1) Omitted

(7.2) Omitted

(7.3) Omitted

(7.4) Omitted

(7.5) Omitted

---

